

1. Electric Charge & Electric Current

- * Charge $Q = ne$ ($e = 1.6 \times 10^{-19} \text{ C}$).
- * Current $I = Q/t$, SI unit: Ampere (A).
- * Direction of current is opposite to flow of electrons.

MIND MAP & IMPORTANT FORMULAS / CONCEPT SUMMARY

- > Ammeter measures current, connected in series, low resistance.
- > 1 Ampere = 1 Coulomb per second.

EXAM BOOSTER & PREVIOUS BOARD QUESTIONS (BSEB / CBSE)

- Q1. Explain the main concept with suitable diagram and units.
- Q2. Write short notes on key phenomena and practical applications.
- Q3. Differentiate between primary principles and real-world examples.
- Q4. Solve numerical questions based on standard Board exam paper patterns.

2. Electric Potential & Potential Difference

- * Work done in moving unit positive charge: $V = W/Q$.
- * SI unit of potential difference: Volt (V).
- * Voltmeter measures V, connected in parallel, high resistance.

MIND MAP & IMPORTANT FORMULAS / CONCEPT SUMMARY

- > 1 Volt = 1 Joule / 1 Coulomb.
- > Cell/battery maintains potential difference across circuit.

EXAM BOOSTER & PREVIOUS BOARD QUESTIONS (BSEB / CBSE)

- Q1. Explain the main concept with suitable diagram and units.
- Q2. Write short notes on key phenomena and practical applications.
- Q3. Differentiate between primary principles and real-world examples.
- Q4. Solve numerical questions based on standard Board exam paper patterns.

3. Ohm Law & V-I Characteristics

- * Statement: $V = IR$ at constant temperature.
- * Resistance $R = V/I$, SI unit: Ohm (Omega).
- * V-I graph for ohmic conductor is a straight line passing through origin.

MIND MAP & IMPORTANT FORMULAS / CONCEPT SUMMARY

- > Slope of V-I graph gives Resistance R .
- > $1 \text{ Ohm} = 1 \text{ Volt} / 1 \text{ Ampere}$.

EXAM BOOSTER & PREVIOUS BOARD QUESTIONS (BSEB / CBSE)

- Q1. Explain the main concept with suitable diagram and units.
- Q2. Write short notes on key phenomena and practical applications.
- Q3. Differentiate between primary principles and real-world examples.
- Q4. Solve numerical questions based on standard Board exam paper patterns.

4. Factors Affecting Resistance & Resistivity

- * Resistance proportional to length ($R \sim l$).
- * Resistance inversely proportional to area ($R \sim 1/A$).
- * Resistivity $\rho = RA/l$, SI unit: Ohm-meter ($\Omega \cdot m$).

MIND MAP & IMPORTANT FORMULAS / CONCEPT SUMMARY

- > Resistivity depends only on material & temperature.
- > Alloys have higher resistivity than pure metals (used in heating coils).

EXAM BOOSTER & PREVIOUS BOARD QUESTIONS (BSEB / CBSE)

- Q1. Explain the main concept with suitable diagram and units.
- Q2. Write short notes on key phenomena and practical applications.
- Q3. Differentiate between primary principles and real-world examples.
- Q4. Solve numerical questions based on standard Board exam paper patterns.

5. Resistors in Series Combination

- * Same current I flows through each resistor.
- * Total Potential Difference $V = V_1 + V_2 + V_3$.
- * Equivalent Resistance $R_s = R_1 + R_2 + R_3$.

MIND MAP & IMPORTANT FORMULAS / CONCEPT SUMMARY

- > Equivalent resistance in series is larger than any individual resistance.
- > If one appliance breaks, whole circuit breaks.

EXAM BOOSTER & PREVIOUS BOARD QUESTIONS (BSEB / CBSE)

- Q1. Explain the main concept with suitable diagram and units.
- Q2. Write short notes on key phenomena and practical applications.
- Q3. Differentiate between primary principles and real-world examples.
- Q4. Solve numerical questions based on standard Board exam paper patterns.

6. Resistors in Parallel Combination

- * Same potential difference V across each resistor.
- * Total Current $I = I_1 + I_2 + I_3$.
- * $1/R_p = 1/R_1 + 1/R_2 + 1/R_3$.

MIND MAP & IMPORTANT FORMULAS / CONCEPT SUMMARY

- > Equivalent resistance in parallel is smaller than smallest individual R .
- > Used in household wiring so each appliance operates independently.

EXAM BOOSTER & PREVIOUS BOARD QUESTIONS (BSEB / CBSE)

- Q1. Explain the main concept with suitable diagram and units.
- Q2. Write short notes on key phenomena and practical applications.
- Q3. Differentiate between primary principles and real-world examples.
- Q4. Solve numerical questions based on standard Board exam paper patterns.

7. Heating Effect of Electric Current

- * Work done $W = VIt = I^2 R t$.
- * Joule Law of Heating: $H = I^2 R t$.
- * Heat produced proportional to I^2 , R , t .

MIND MAP & IMPORTANT FORMULAS / CONCEPT SUMMARY

- > Applications: Electric Iron, Heater, Toaster, Fuse wire.
- > Fuse wire has low melting point & high resistance.

EXAM BOOSTER & PREVIOUS BOARD QUESTIONS (BSEB / CBSE)

- Q1. Explain the main concept with suitable diagram and units.
- Q2. Write short notes on key phenomena and practical applications.
- Q3. Differentiate between primary principles and real-world examples.
- Q4. Solve numerical questions based on standard Board exam paper patterns.

8. Electric Power & Commercial Unit of Energy

- * Electric Power $P = W/t = VI = I^2 R = V^2 / R$.
- * SI unit of Power: Watt (W) = 1 Joule/second.
- * Commercial Unit: 1 kilowatt-hour (1 kWh) = 3.6×10^6 Joules.

MIND MAP & IMPORTANT FORMULAS / CONCEPT SUMMARY

- > 1 kWh is called 1 Unit of electricity.
- > Power rating (e.g. 100W, 220V) indicates energy consumption rate.

EXAM BOOSTER & PREVIOUS BOARD QUESTIONS (BSEB / CBSE)

- Q1. Explain the main concept with suitable diagram and units.
- Q2. Write short notes on key phenomena and practical applications.
- Q3. Differentiate between primary principles and real-world examples.
- Q4. Solve numerical questions based on standard Board exam paper patterns.

9. Important Circuit Diagrams & Numericals

- * Series vs Parallel connection circuit schematics.
- * Calculating total current & power in complex circuits.
- * Solving board exam numerical problems step-by-step.

MIND MAP & IMPORTANT FORMULAS / CONCEPT SUMMARY

- > Always convert time to seconds in $H = I^2 R t$ formula.
- > Power $P = V^2 / R$ when appliances are in parallel across same V .

EXAM BOOSTER & PREVIOUS BOARD QUESTIONS (BSEB / CBSE)

- Q1. Explain the main concept with suitable diagram and units.
- Q2. Write short notes on key phenomena and practical applications.
- Q3. Differentiate between primary principles and real-world examples.
- Q4. Solve numerical questions based on standard Board exam paper patterns.

10. One Page Quick Revision & Exam Booster

- * All key formulas: $Q=ne$, $I=Q/t$, $V=W/Q$, $V=IR$, $\rho=RA/l$, $P=VI$, $H=I^2Rt$.
- * Definitions, SI units, and conversion factors.
- * Previous 5 Years Board Exam Questions (BSEB Class 10).

MIND MAP & IMPORTANT FORMULAS / CONCEPT SUMMARY

- > Series vs Parallel comparative table.
- > Memory tricks for Ohm Law and Power formulas.

EXAM BOOSTER & PREVIOUS BOARD QUESTIONS (BSEB / CBSE)

- Q1. Explain the main concept with suitable diagram and units.
- Q2. Write short notes on key phenomena and practical applications.
- Q3. Differentiate between primary principles and real-world examples.
- Q4. Solve numerical questions based on standard Board exam paper patterns.